

8. Foundations of processor design: combinational logic

EECS 370 – Introduction to Computer Organization – Winter 2015


Robert Dick, Andrew Lukefahr, and Satish Narayanasamy

**EECS Department
University of Michigan in Ann Arbor, USA**

© Dick-Lukefahr-Narayanasamy, 2015

The material in this presentation cannot be
copied in any form without our written permission

Recap: Floating Point Representation

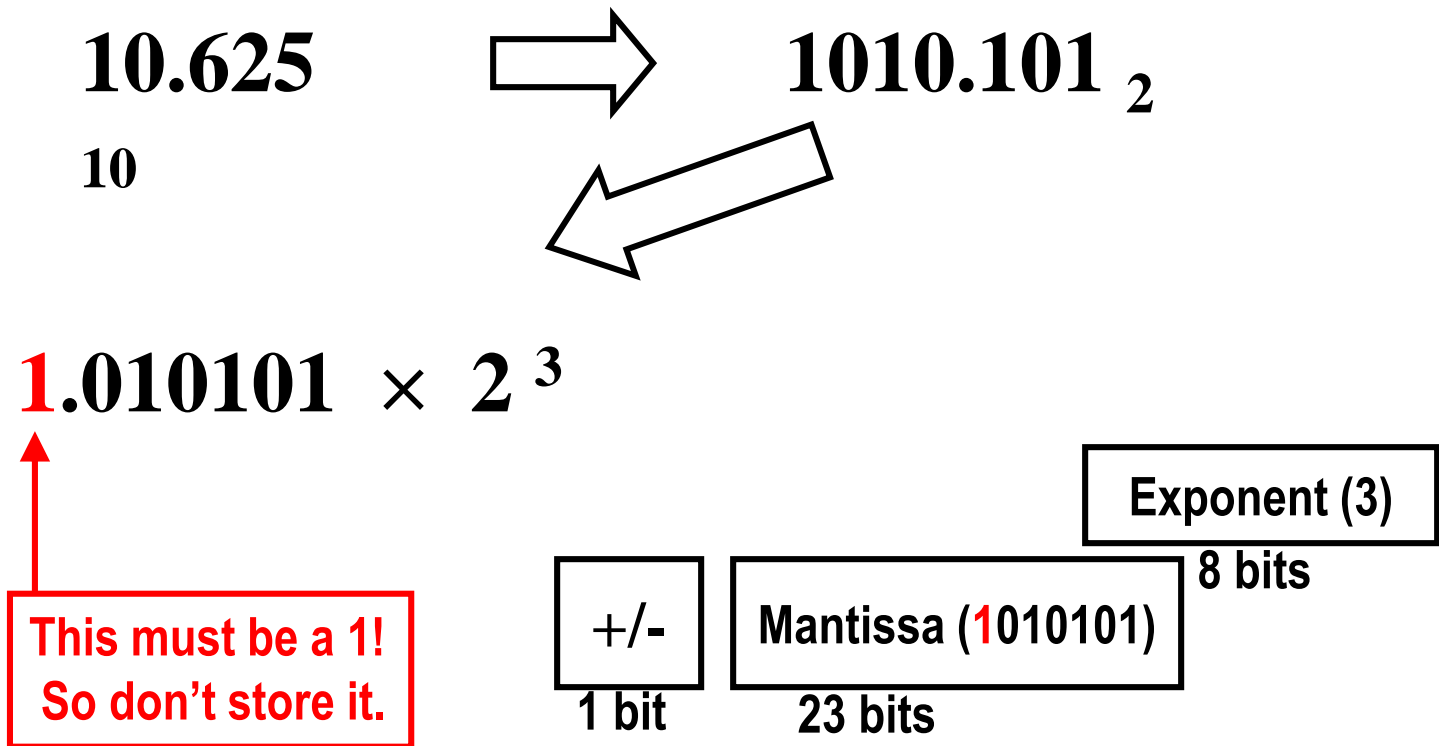

$$10.625_{10} = 0 \ 10000010 \ 010101000000000000000000$$

Next 3 Lectures

1. Combinational Logic:

- Basics of electronics; logic gates, muxes, decoders

1. Sequential Logic

- Clocks, latches and flip-flops

2. State Machines

- Building a simple processor

Levels of abstraction

- ❑ Quantum level, solid state physics
- ❑ Conductors, Insulators, Semiconductors.
- ❑ Doping silicon to make diodes and transistors.
- ❑ Building simple gates, boolean logic, and truth tables
- ❑ Combinational logic: muxes, decoders
- ❑ Clocks
- ❑ Sequential logic: latches, memory
- ❑ State machines
- ❑ Processor Control: Machine instructions
- ❑ Computer Architecture: Defining a set of instructions


Start with the materials: Conductors and Insulators

- ❑ **Conductor**: a material that permits electrical current to flow easily. (low resistance to current flow)
 - Lattice of atoms with free electrons

- ❑ **Insulator**: a material that is a poor conductor of electrical current (High resistance to current flow)
 - Lattice of atoms with strongly held electrons

- ❑ **Semi-conductor**: a material that can act like a conductor or an insulator depending on conditions. (variable resistance to current flow)

 Goal: a switch that controls other switches



Doped silicon semiconductors

- ❑ How do we make tiny electronically controlled switches?
 - Semiconductors: control whether it conducts or not
- ❑ Basic semiconductor material of most electronics
- ❑ Start with pure crystalline silicon (4 valence electrons)
- ❑ Deliberately add a **small** amount of an impurity with a different number of valence electrons
 - Light doping: 1 in 100,000,000 atoms
 - Heavy doping: 1 in 10,000 atoms
- ❑ This small amount of impurity can drastically change the electrical properties of the silicon!

N and P types

□ N-type


- Add atoms of something with 5 valence electrons, such as phosphorus
- Crystal ends up with some extra relatively free electrons
- These free electrons can move to carry current

□ P-type

- Add atoms of something with 3 valence electrons, such as boron
- Crystal ends up with some missing electrons (holes)
- Moving holes can also carry current

Using doped silicon to make a junction diode

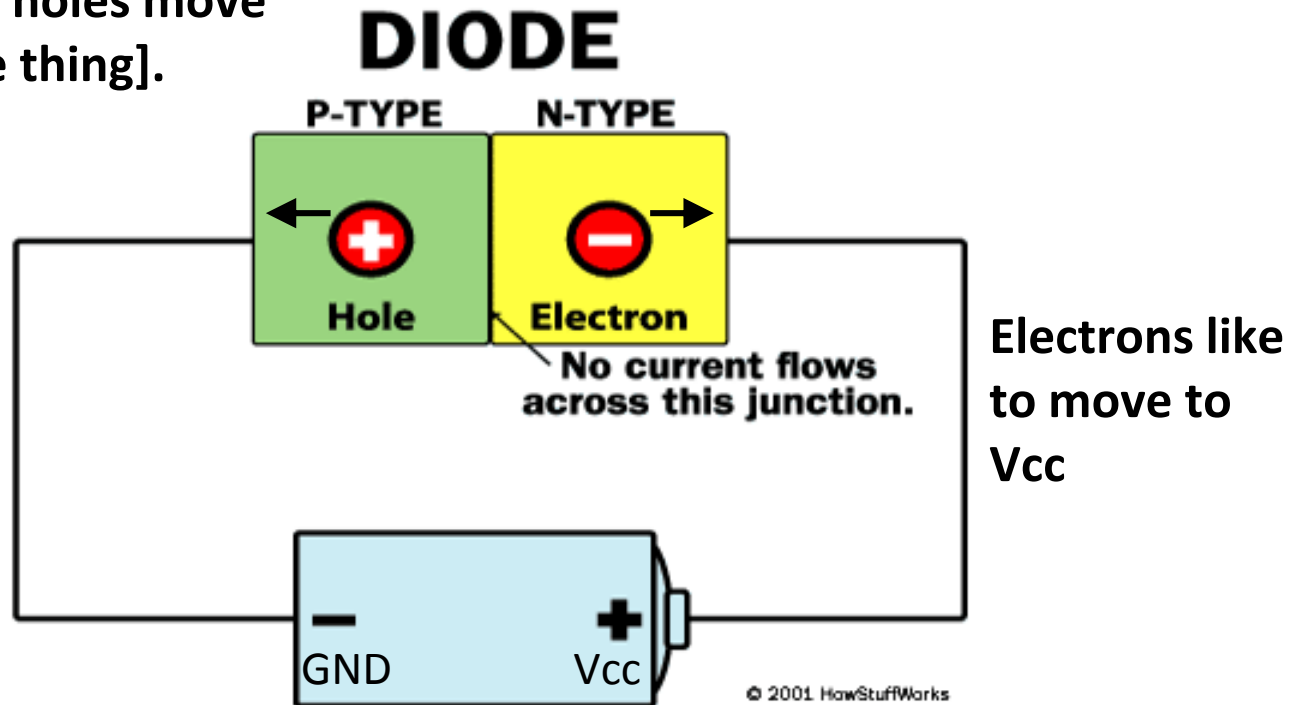
Electrons move from GND to fill holes [or holes move to GND – same thing].



No current flows across the p-n junction

Using doped silicon to make a junction diode

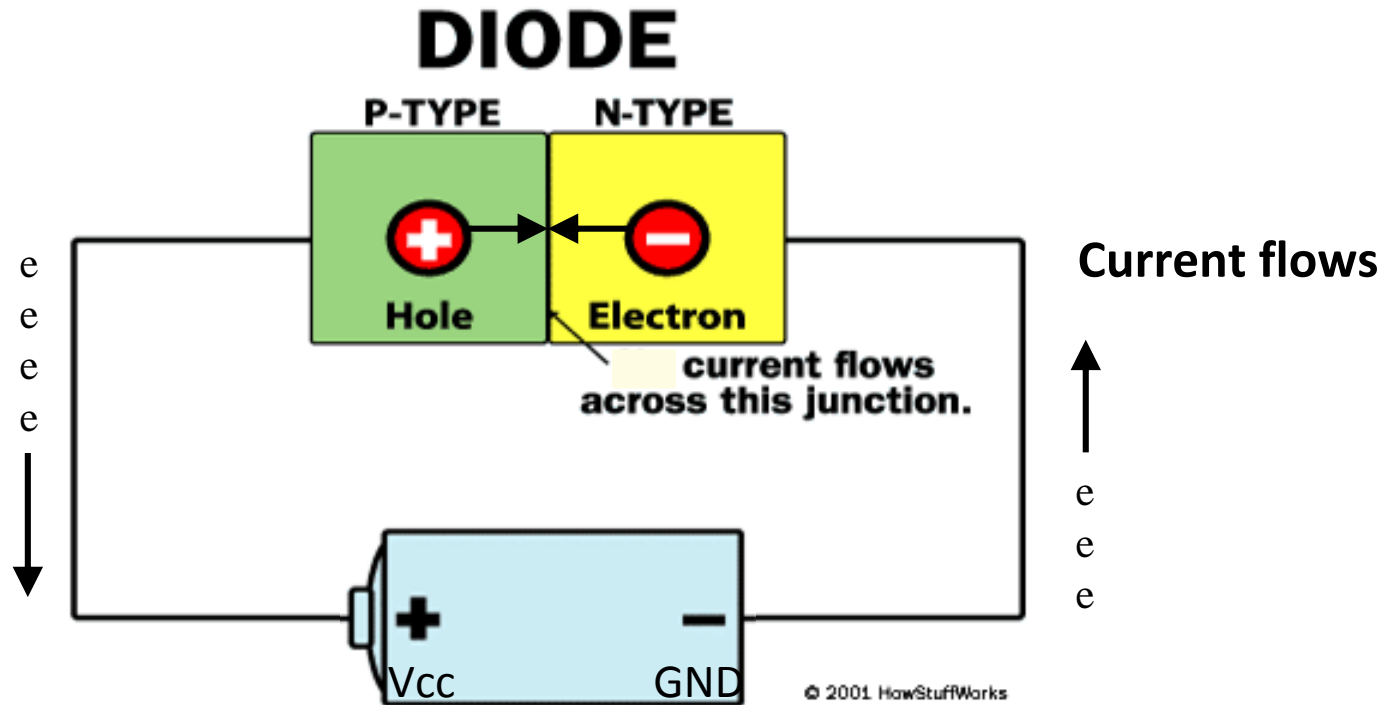
A junction diode allows current to flow in one direction and blocks it in the other.




Current flows across the p-n junction

Making a transistor

 Our first level of abstraction is the transistor (basically 2 diodes sitting back-to-back)




 Electrical engineers use a diagram like this:



Making a transistor

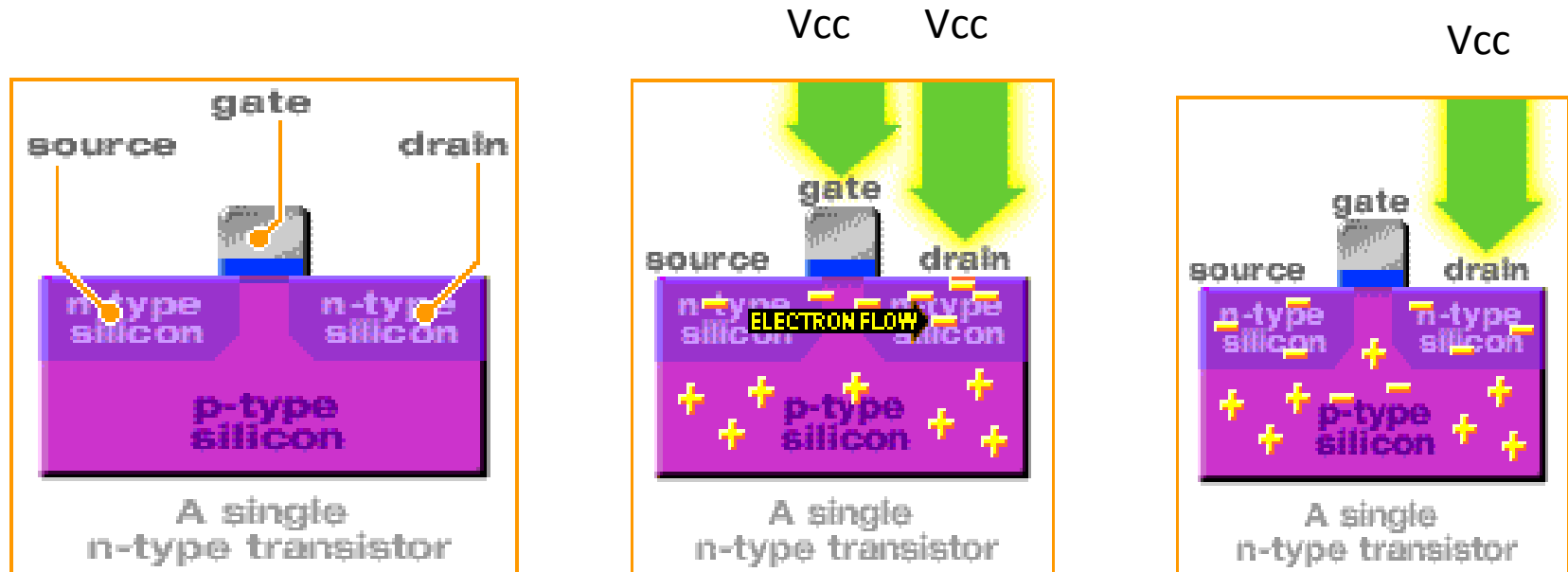Transistors are electronic switches connecting the source to the drain if the gate is “on”.



<http://www.intel.com/education/transworks/INDEX.HTM>

Recent pictures and the near future

Source: Intel

gate


Today

drain


Future

source


50nm

 

 
50nm transistor dimension is ~2000x smaller than diameter of human hair



30nm

 

20nm

 

15nm

90nm technology
2003


65nm technology 2005

45nm technology
2008


32nm technology
2010

The future carries a lot of problems..


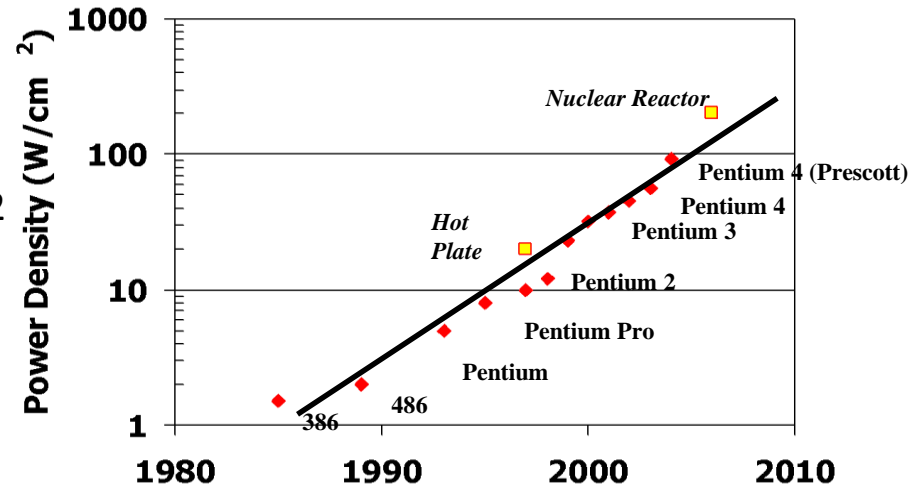
- ❑ *Area is NOT one of them*
- ❑ Power density – Watts/mm²
- ❑ Reliability (faults)




interconnect

 

via

  


transients

 

Testing burn-in

- ❑ Process variation (not all transistors are equal)
- ❑ ...

As for power: Cooking-aware Computing

 

Source: The New York Times, 25 June 2002


Basic gate: Inverter

CS abstraction - logic function


Truth Table

I	O
0	1
1	0

Schematic symbol (CS/EE)

 

Transistor-level schematic

 

CMOS Water Analogy

Electron: water molecule

Charge: weight of water

Voltage: height



Current: flow rate

Capacitance: container cross-section

(Think of power-plants that store energy in water towers)

Slide courtesy D. Brooks, Harvard

Liquid Inverter

  

- ❑ Capacitance at input
 - Gates of NMOS, PMOS
 - Metal interconnect
- ❑ Capacitance at output
 - Fanout (# connections) to other gates
 - Metal Interconnect

NMOS conducts when water level is above switching threshold


PMOS conducts below

No conduction after container full


Slide courtesy D. Brooks, Harvard

Inverter Signal Propagation (1)

$t < 0$
 $V_{in} = 0$

 


$t = 0$
 $V_{in} = 1$

 

Slide courtesy D. Brooks, Harvard

Inverter Signal Propagation (2)

 


Slide courtesy D. Brooks, Harvard


Basic gate: NAND (like the LC-2K NAND)

Truth Table


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 

Transistor-level schematic

 


Layout schematic

 

Basic gates: AND and OR


AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 

OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 


Exercise

- ❑ NAND can be used to implement *all* other logic functions!
- ❑ Exercise:
- ❑ Implement INV using only NAND gates
- ❑ Implement AND using only NAND gates
- ❑ Implement OR using only NAND gates
- ❑ Implement XOR using only NAND gates

Basic gate: XOR (eXclusive OR)

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

 


Exercise


❑ INV




❑ AND

 

❑ OR

 


❑ XOR

 


Combinational Circuits implement Boolean expressions

- ❑ Output is determined exclusively by the input
- ❑ **No memory**: Output is valid only as long as input is
 - Adder is the basic gate of the ALU (Lecture 9)
 - Decoder is the basic gate of indexing
 - MUX is the basic gate controlling data movement


Half Adder

 

Decoder

 

MUX

 

- ❑ Exercise: write the truth tables for each of these

Half Adder


- ❑ Carry bit (C) can use an AND gate
- ❑ Sum bit (S) can use an XOR gate

Truth Table

Add 2 1-bit numbers

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Circuit

 

Decoder

A ₁	A ₀	Out
0	0	0
0	1	0
1	0	0
1	1	1

Out₃ is just an AND gate

A ₁	A ₀	Out
0	0	0
0	1	0
1	0	1
1	1	0

Out₂ would be an AND gate if A₀ was inverted

A ₁	A ₀	Out
0	0	0
0	1	1
1	0	0
1	1	0

Invert
A₁

A ₁	A ₀	Out
0	0	1
0	1	0
1	0	0
1	1	0


Invert A₁ and A₂

Truth Table

Select a single line
given an index

A ₁	A ₀	Out ₃₋₀
0	0	0001
0	1	0010
1	0	0100
1	1	1000


Circuit

 

Multiplexor (MUX)

- ❑ Input S selects either input A or input B
- ❑ This is called a 2x1 MUX, since it has 2 inputs and 1 output

Circuit

 

Truth Table


Select one of multiple input lines to pass to the output

A	B	S	C
a	b	0	a
a	b	1	b


Exercise

- ❑ Build (draw) a 4x1 mux
- ❑ Hint: use 2x1 muxes

Circuit

 


Symbol

 


Exercise

- 4x1 mux made from 2x1 muxes

 


Symbol

 


Building combinational circuits: Half and Full adder

Half Adder


A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

Full Adder

 


8-bit Ripple Carry Adder

 


Unfortunately this has a very large propagation time for 32 or 64 bit adds

One more problem: Propagation delay in combinational gates

 - ❑ Gate outputs do not change exactly when inputs do.
 - Transmission time over wires (\sim speed of light)
 - Saturation time to make transistor gate switch
- \Rightarrow Every combinatorial circuit has a propagation delay (time between input and output stabilization)



Timing in Combinational Circuits

 


What is the input/output delay (or simply, delay) of the MUX?

Waveform viewers are part of designers' daily life




What is the delay of this Circuit?

 Each oval represents one gate,
the type does not matter



 
Exercise

- ❑ Use the blocks we have learned about so far (full adder, NAND, mux) to build this circuit
 - Input A, 32 bits
 - Input B, 32 bits
 - Input S, 1 bit
 - Output, 32 bits
 - When S is low, the output is $A+B$, when S is high, the output is $\text{NAND}(a,b)$
- ❑ Hint: you can express multi-bit gates like this:



 
Exercise

- ❑ This is a basic ALU (Arithmetic Logic Unit)
- ❑ It is the heart of a computer processor!




LC-2K ALU

Circuit

 

Symbol


 


Verifying a Circuit

❑ How many possible inputs are there for a 2-1 mux?

❑ How many possible inputs are there for a Core i7 with a 1,366 pins? For simplicity, assume all the pins are inputs.

  
❑ How long would it take to try them all?



Verifying a Circuit

❑ How many possible inputs are there for a 2-1 mux?

 - A, B, or C could be 0 or 1, so $2^3 = 8$
- Easy to test all possible inputs




❑ How many possible inputs are there for a Core i7 with a 1,366 pins? For simplicity, assume all the pins are inputs.

- $2^{1366} = \text{REALLY BIG NUMBER}$
- Comparison: $\sim 10^{80} = 2^{266}$ atoms in the universe

❑ How long would it take to try them all?

- We don't have enough time!

 

Verifying a Circuit

- ❑ It's hard to verify combinational circuits
- ❑ *It gets worse when we add memory to the circuit*
- ❑ Next time: sequential circuits