

9. Foundations of processor design: memory elements

EECS 370 – Introduction to Computer Organization – Winter 2015

Robert Dick, Andrew Lukefahr, and Satish Narayanasamy

**EECS Department
University of Michigan in Ann Arbor, USA**


© Dick-Lukefahr-Narayanasamy, 2015

The material in this presentation cannot be
copied in any form without our written permission


Recap: Combinational Circuits – implement Boolean expressions

- ❑ **No memory:** Output a function only of input
 - ❑ Undefined input implies undefined output
- Adder is the basic gate of the ALU
 - Decoder is the basic gate of indexing
 - MUX is the basic gate controlling data movement


Half Adder

 

Decoder

 

MUX

 


Recap:


Building combinational circuits: Half and Full adder

Half Adder

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 


Full Adder

 


Next topic:

Sequential logic: giving memory to circuits

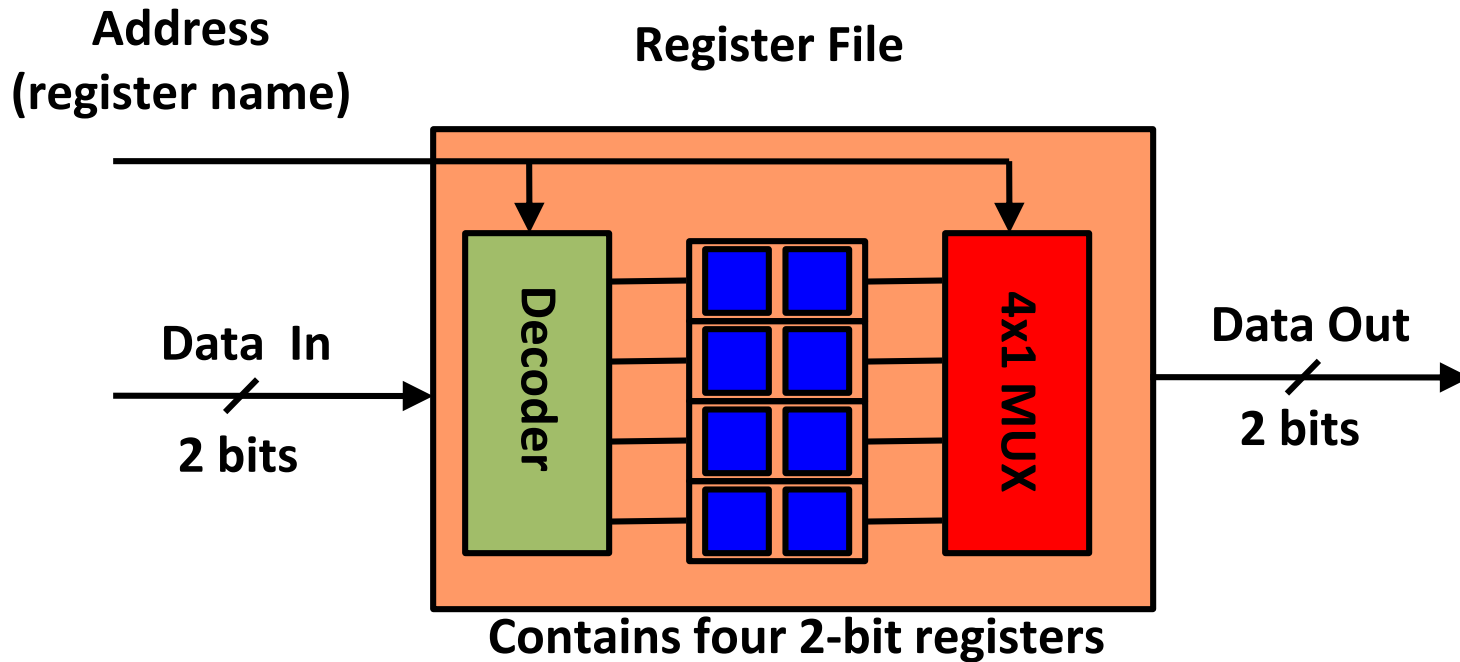Why do they need memory – Example: register file




Let's look at the following circuit

 

What is the value of Q if \bar{R} is 1 and \bar{S} is 0?


Building the Truth Table

 

\bar{S}	\bar{R}	Q	\bar{Q}
0	1	1	0
1	0	0	1

What is the value of Q if \bar{R} is 0 and \bar{S} is 1?


For a Basic Memory Cell

 

What is the value of Q if \bar{R} is 1 and \bar{S} is 1?


As long as R and S remain 1 then the value Q (and \bar{Q}) will remain unchanged. This value is **stored** in this circuit. **This is a basic memory cell.**

With unstable inputs 0,0

 

What is the value of Q if \bar{R} is 0 and \bar{S} is 0?

Transparent D Latch

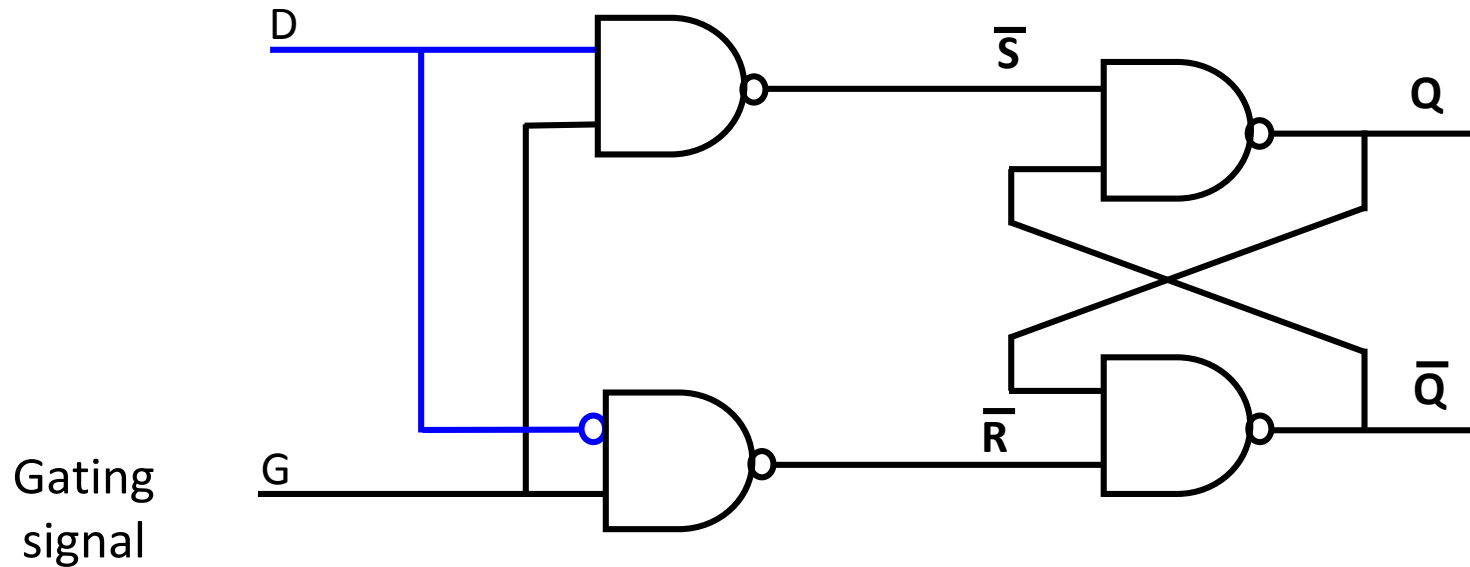

	D	G	Q	\bar{Q}	
	0	0	Q	\bar{Q}	Set state is retained
	0	1	0	1	
Next state is set	1	0	Q	\bar{Q}	
	1	1	1	0	

Q?

D



G



Q

Adding a clock to the mix

- ❑ We can design more interesting circuits if we have a clock signal
- ❑ The use of a clock enables a sequential circuit to **predictably** change state (and store information).
- ❑ A clock signal alternates between 0 and 1 states at a fixed frequency (e.g., 100MHz)
- ❑ What should the clock frequency be?

Clocks

□ Clock signal


- Periodic pulse
- Generated using oscillating crystal or ring oscillator
- Distributed throughout chip using clock distribution net



□ With clock signals we can create a new class of circuits called **sequential**

- Output determined by inputs & **previous** state

Edge Triggered D Flip-flop

 

Q?

Data




Clock




Q

Why edge-triggered flip-flops?

 

IS LIKE A TOLL-GATE


 


IS LIKE AN AIR-LOCK

In edge-triggered flip-flops, the latching edge provides convenient abstraction of “instantaneous” change of state.


Tri-state Logic

  - ❑ The output of a gate can be any of **three** different states:
one, zero or not connected
 - Need to disconnect the circuit. How?




Implemented as
a single transistor


A Static Memory Cell

 


A 4-Bit Register

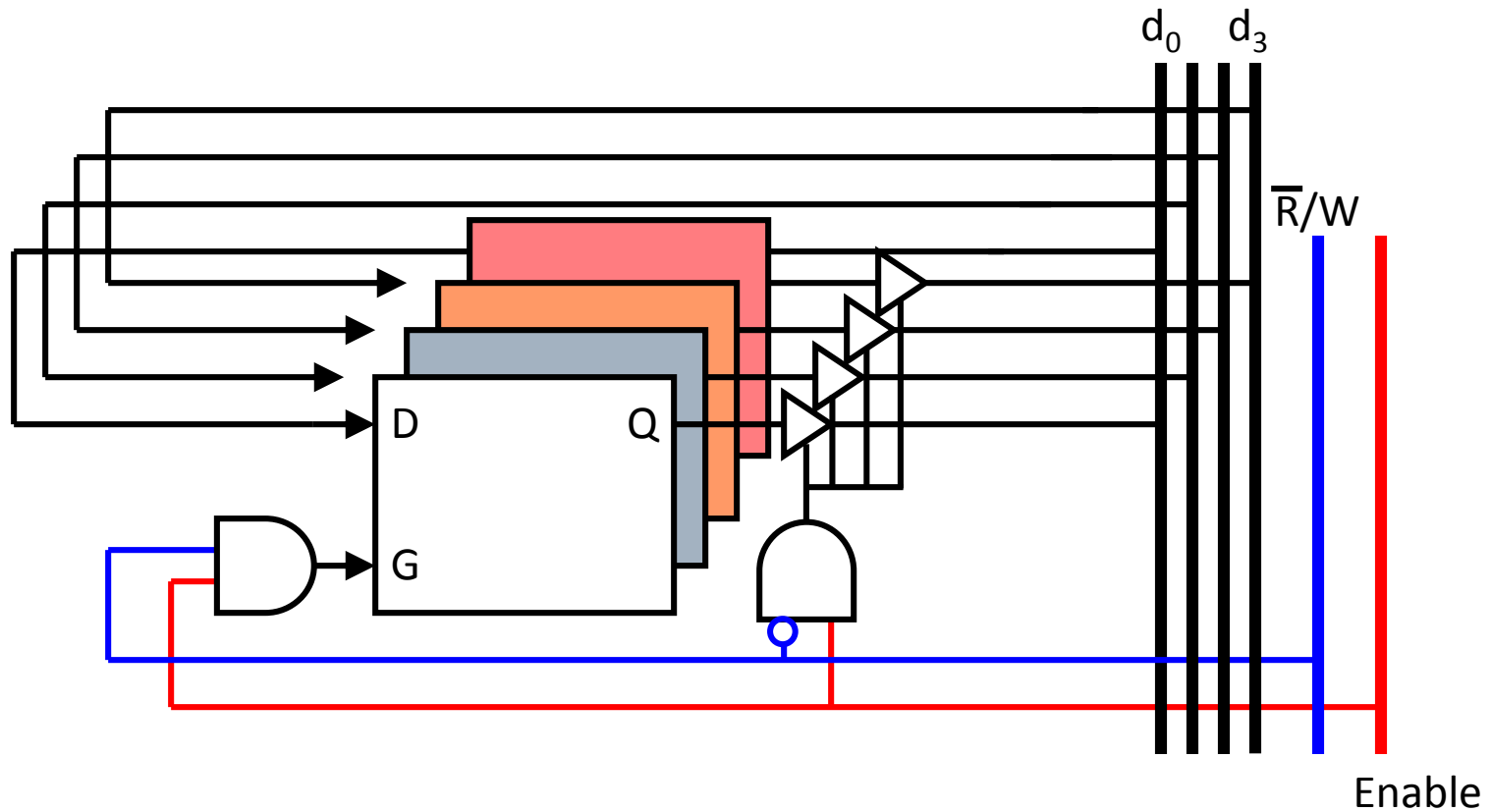

Addressing Memory Arrays

 

A Scheme with Fewer Components

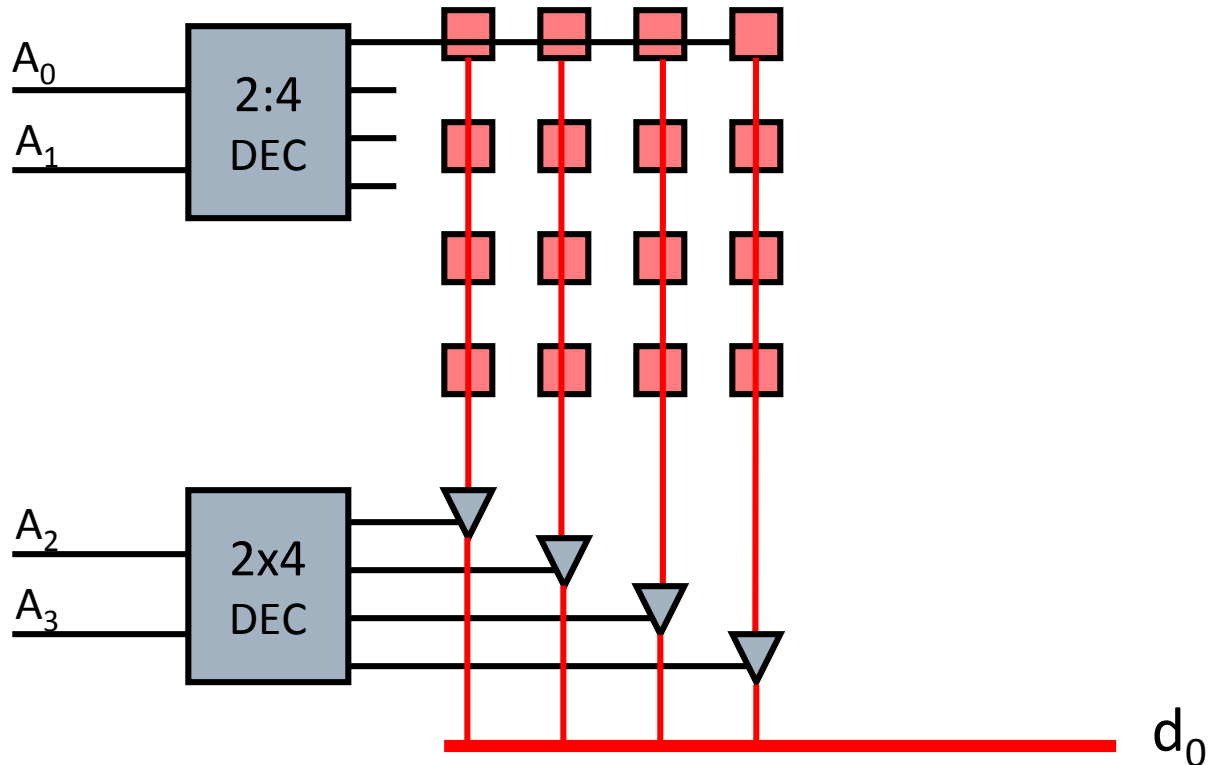

16 X 1 BIT MEMORY

Putting it in a package



18-bit X 2M MEMORY (36 MBits)

Other Memories

❑ Static RAM

- Built from sequential circuits
 - Takes 4-6 transistors to store 1 bit
 - Fast access (< 1 ns access possible)

❑ Dynamic RAM

- Built using a single transistor and a capacitor
 - 1's must be refreshed often to retain value
 - Slower access than static RAM
 - Much more dense layout than static RAM

❑ ROM, PROM, Flash memory, etc. ➡ Later

